


CSE331 Assignment Report

Ahmed Semih Özmekik

XOR

Simple circuit shown here implemented.

 
```
module gate_xor(c, a, b);  
  
input a, b;  
wire a_not, b_not, a_or_b, anot_or_bnot;  
output c;  
  
// inverting  
not a_NOT(a_not, a);  
not b_NOT(b_not, b);  
  
or or0(a_or_b, a, b);  
or or1(anot_or_bnot, a_not, b_not);  
  
and xor_result(c, a_or_b, anot_or_bnot);  
endmodule
```



4x1 MUX

Simple circuit shown here implemented.¹

```
module mux_4X1(y, s0, s1, i0, i1, i2, i3);  
  
input s0, s1, i0, i1, i2, i3; // two selection  
output y; // one output Y  
  
// middle wires  
wire s0_not, s1_not;  
wire and0, and1, and2, and3;  
  
// inverting  
not s0_NOT(s0_not, s0);  
not s1_NOT(s1_not, s1);  
  
and s0_s1_i3(and0, s0, s1, i3);  
and s0not_s1_i2(and1, s0_not, s1, i2);  
and s0_s1not_i1(and2, s0, s1_not, i1);  
and s0not_s1not_i0(and3, s0_not, s1_not, i0);  
  
or mux_result(y, and0, and1, and2, and3);  
endmodule
```

 

¹ C's are being S's in our case, i.e. S0<-C0, S1<-C1, so on.


1-bit ALU

```
gate_xor get_b_real(b_real, b, alu_op[2]); 1
// nots
not i0not(i0_not, i0); 4
not level1andnot(level1_and_not, level1_and); 9
// ands
and level0and(level0_and, i0_not, i1); 5
and level1and(level1_and, level0_and, c_in); 6

or level0or(level0_or, level0_and, c_in); 7

and get_i0(i0, a, b_real); // i0 = and 2
or get_i1(i1, a, b_real); // i1 = or 3
and get_i2(i2, level1_and_not, level0_or); // i2 = (add / sub) 10

 
// carry_out
or get_c_out(c_out, level1_and, i0); 8
// result 11
mux_4X1 alu_result(r, alu_op[0], alu_op[1], i0, i1, i2, less);
```



1-bit ALU for MSB

Only the different extra parts shown.
 
```
// msb parts
gate_xor getV(v, c_in, c_out); 1
gate_xor getless(set, v, i2); 1
```



32-bit ALU

As shown with 3 dots, it comes from LSB and continues 'til MSB.

```
alu_1bit gen_29thALU(a[29], b[29], c[28], 0, alu_op, r[29], c[29]);
alu_1bit gen_30thALU(a[30], b[30], c[29], 0, alu_op, r[30], c[30]);
msb_alu_1bit gen_31thALU(a[31], b[31], c[30], 0, alu_op, r[31], c_out, v, set);
```

And comes from first level of OR's and continues 'til 4th level.

```
// Level 3 or's
or level3or0(level3_or[0], level2_or[0], level2_or[1]);
or level3or1(level3_or[1], level2_or[2], level2_or[3]);

// Level 4 or's
or level4or(level4_or, level3_or[0], level3_or[1]);

not result(z, level4_or);
```

XOR

Every combinations tested.

```
# time - 0, a -0,b-0, c-0
# time - 20, a -0,b-1, c-1
# time - 40, a -1,b-0, c-1
# time - 60, a -1,b-1, c-0
```

4x1 MUX

As shown below, in each one different bit positions set and *mux* chooses the correct one.

```
# time - 0, input - 0001, s0-0, s1-0, y-1
# time - 20, input - 0010, s0-0, s1-1, y-1
# time - 40, input - 0100, s0-1, s1-0, y-1
# time - 60, input - 1000, s0-1, s1-1, y-1
```

1-bit ALU

Every –valid– combinations tested.

AND	<pre># time - 0, a -0, b-0, c_in-0, alu-000, r-0, c_out-0 # time - 20, a -0, b-1, c_in-0, alu-000, r-0, c_out-0 # time - 40, a -1, b-0, c_in-0, alu-000, r-0, c_out-0 # time - 60, a -1, b-1, c_in-0, alu-000, r-1, c_out-1 # time - 80, a -0, b-0, c_in-0, alu-001, r-0, c_out-0 # time - 100, a -0, b-1, c_in-0, alu-001, r-1, c_out-0 # time - 120, a -1, b-0, c_in-0, alu-001, r-1, c_out-0 # time - 140, a -1, b-1, c_in-0, alu-001, r-1, c_out-1 # time - 160, a -0, b-0, c_in-0, alu-010, r-0, c_out-0 # time - 180, a -0, b-1, c_in-0, alu-010, r-1, c_out-0 # time - 200, a -1, b-0, c_in-0, alu-010, r-1, c_out-0 # time - 220, a -1, b-1, c_in-0, alu-010, r-0, c_out-1 # time - 240, a -0, b-0, c_in-1, alu-010, r-1, c_out-0 # time - 260, a -0, b-1, c_in-1, alu-010, r-0, c_out-1 # time - 280, a -1, b-0, c_in-1, alu-010, r-0, c_out-1 # time - 300, a -1, b-1, c_in-1, alu-010, r-1, c_out-1 # time - 320, a -0, b-0, c_in-1, alu-110, r-0, c_out-1 # time - 340, a -0, b-1, c_in-1, alu-110, r-1, c_out-0 # time - 360, a -1, b-0, c_in-1, alu-110, r-1, c_out-1 # time - 380, a -1, b-1, c_in-1, alu-110, r-0, c_out-1 # time - 400, a -0, b-0, c_in-1, alu-111, r-0, c_out-1 # time - 420, a -0, b-1, c_in-1, alu-111, r-1, c_out-0 # time - 440, a -1, b-0, c_in-1, alu-111, r-0, c_out-1 # time - 460, a -1, b-1, c_in-1, alu-111, r-0, c_out-1</pre>
OR	
ADD	
SUBSTRACT	
LESS	

1-bit ALU for MSB

Parts which are not shown is same as with 1-bit ALU, because circuit is copied and pasted, overflow and set bits added to end of the circuit in which tested below.

ADD	<pre># time - 0, a -0, b-0, c_in-0, alu-010, r-0, c_out-0, v-0, set-0 # time - 20, a -0, b-1, c_in-0, alu-010, r-1, c_out-0, v-0, set-1 # time - 40, a -1, b-0, c_in-0, alu-010, r-1, c_out-0, v-0, set-1 # time - 60, a -1, b-1, c_in-0, alu-010, r-0, c_out-1, v-1, set-1 # time - 80, a -0, b-0, c_in-1, alu-010, r-1, c_out-0, v-1, set-0 # time - 100, a -0, b-1, c_in-1, alu-010, r-0, c_out-1, v-0, set-0 # time - 120, a -1, b-0, c_in-1, alu-010, r-0, c_out-1, v-0, set-0 # time - 140, a -1, b-1, c_in-1, alu-010, r-1, c_out-1, v-0, set-1 # time - 160, a -0, b-0, c_in-1, alu-110, r-0, c_out-1, v-0, set-0 # time - 180, a -0, b-1, c_in-1, alu-110, r-1, c_out-0, v-1, set-0 # time - 200, a -1, b-0, c_in-1, alu-110, r-1, c_out-1, v-0, set-1 # time - 220, a -1, b-1, c_in-1, alu-110, r-0, c_out-1, v-0, set-0</pre>
SUBSTRACT	

32-bit ALU

Tests are shown with separate shots of same output. Since *ModelSim* does not print (-) sign before negative numbers (calculates and shows the number properly), I put a small line to indicate (-) sign in the last picture.

AND	<pre># time - 0, alu-000, a: 0x11111111111111111111111111111111, b: 0x00000000000000000000000000000010, # time - 20, alu-000, a: 0x11111111111111111111111111111111, b: 0x00000000000000000000000000000111, # time - 40, alu-001, a: 0x00000000000000000000000000000001001, b: 0x000000000000000000000000000001010, # time - 60, alu-001, a: 0x11111111111111111111111111111111, b: 0x000000000000000000000000000000000, # time - 80, alu-010, a: 0x0000000000000000000000000000000011, b: 0x0000000000000000000000000000011010, # time - 100, alu-010, a: 0x11111111111111111111111111111111, b: 0x000000000000000000000000000000011110, # time - 120, alu-110, a: 0x000000000000000000000000000000001101, b: 0x000000000000000000000000000000011, # time - 140, alu-110, a: 0x00000000000000000000000000000001001, b: 0x00000000000000000000000000000001010, # time - 160, alu-110, a: 0x0000000000000000000000000000000111, b: 0x000000000000000000000000000000011010, # time - 180, alu-111, a: 0x1000000000000000000000000000000011, b: 0x000000000000000000000000000000011010,</pre>
OR	
ADD	
SUBSTRACT	
LESS	

AND	<pre>r: 0x00000000000000000000000000000000010 c_out:1, r: 0x000000000000000000000000000000000111 c_out:1, r: 0x00000000000000000000000000000000011011 c_out:0, r: 0x1111111111111111111111111111111111 c_out:0, r: 0x00000000000000000000000000000000011101 c_out:0, r: 0x0000000000000000000000000000000001101 c_out:1, r: 0x0000000000000000000000000000000001010 c_out:1, r: 0x1111111111111111111111111111111110111 c_out:1, r: 0x11111111111111111111111111111111101101 c_out:0, r: 0x0000000000000000000000000000000001 c_out:1,</pre>
OR	
ADD	
SUBSTRACT	
LESS	

AND	<pre>a: 1, b: 2, r: 2, v:0, z:0 a: 1, b: 7, r: 7, v:0, z:0 a: 9, b: 18, r: 27, v:0, z:0 a: 1, b: 0, r: 1, v:0, z:0 a: 3, b: 26, r: 29, v:0, z:0 , a: 1, b: 14, r: 13, v:0, z:0 , a: 13, b: 3, r: 10, v:0, z:0 , a: 9, b: 18, r: -9, v:0, z:0 , a: 7, b: 26, r: -19, v:0, z:0 , a: 2147483645, b: 26, r: 1, v:1, z:0</pre>
OR	
ADD	
SUBSTRACT	
LESS	

Number of Logic Gates

The number of logic gates I have used is shown below with my calculation. (only NOT, AND, OR gates used and counted.)

$$\begin{aligned}\text{XOR} &= 2*(\text{NOT}) + 2*(\text{OR}) \\ &= 4\end{aligned}$$

$$\begin{aligned}\text{4x1 MUX} &= 2*(\text{NOT}) + 4*(\text{AND}) + 1*(\text{OR}) \\ &= 7\end{aligned}$$

$$\begin{aligned}\text{1-bit ALU} &= 2*(\text{NOT}) + 4*(\text{AND}) + 3*(\text{OR}) + 1*(\text{MUX}) \\ &= 16\end{aligned}$$

$$\begin{aligned}\text{1-bit ALU for MSB} &= (\text{1-bit ALU}) + 2*(\text{XOR}) \\ &= 24\end{aligned}$$

$$\begin{aligned}\text{32-bit ALU} &= 31*(\text{1-bit ALU}) + 1*(\text{1-bit ALU MSB}) + (4 \text{ LEVEL OR})^2 + 1*(\text{NOT}) \\ &= 31*16 + 1*24 + 31 + 1 \\ &= 552\end{aligned}$$

$$\text{Total Gates} = 552$$

$$2^{(4 \text{ LEVEL OR})} = 2^4 + 2^3 + 2^2 + 2^1 + 2^0$$